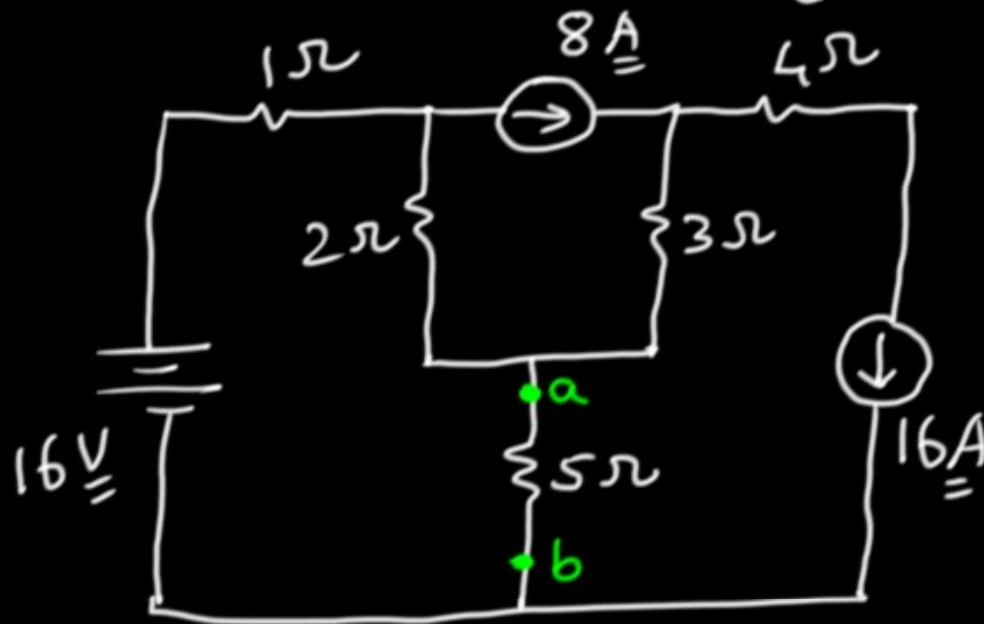


Tvs


# Network Analysis [Day-10]




1] Determine power absorbed by  $5\Omega$  resistance using Thevenin & Norton Theorem.



a) T.T  
S-I  $R_{TH}$

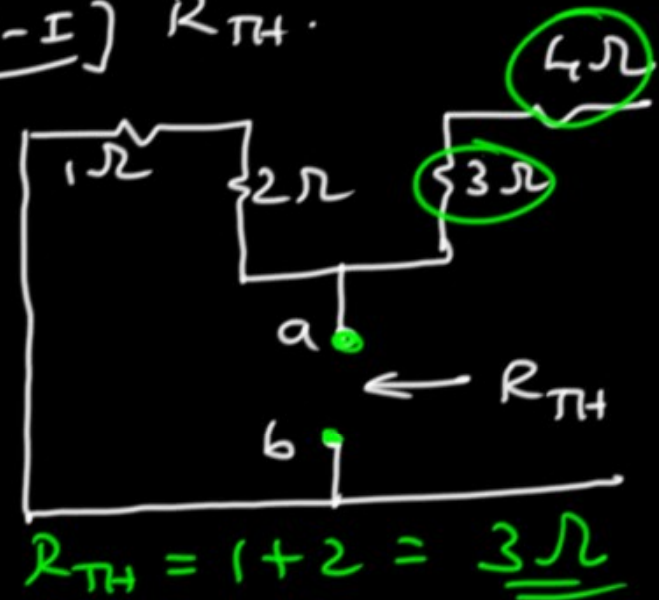


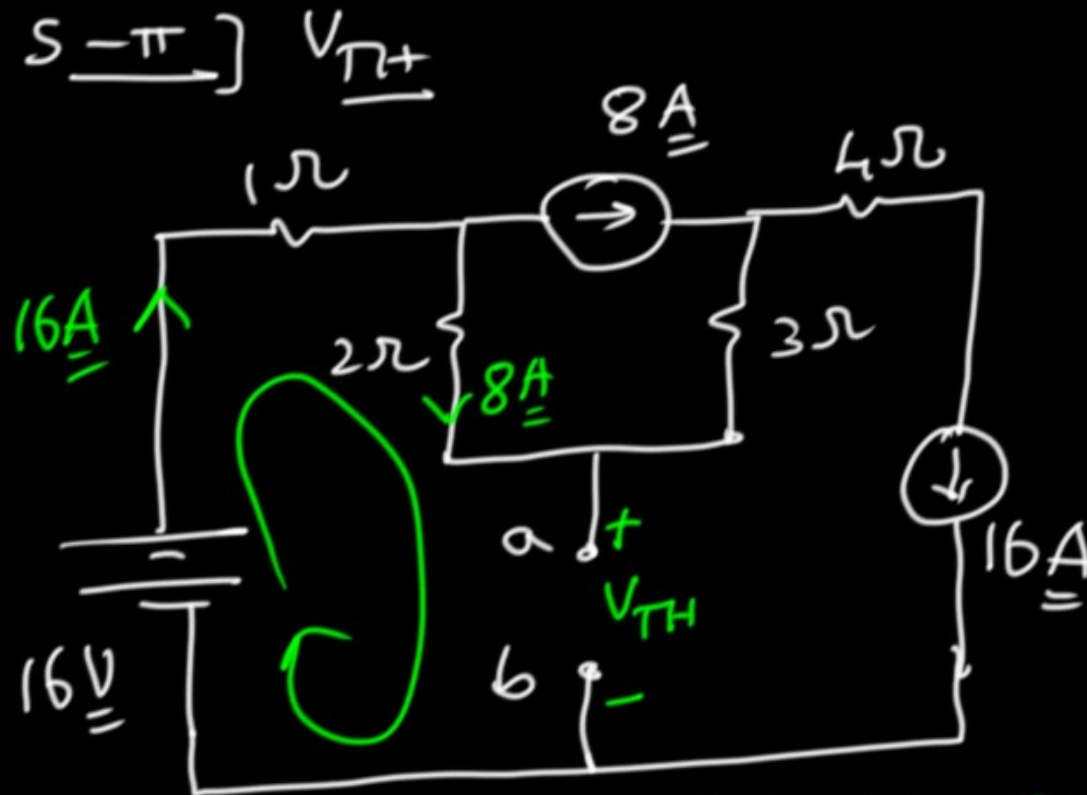

KCL + KVL

$$-16 + 16(1) + 8(2) + V_{TH} = 0$$

$$V_{TH} = -16 \text{ Volts}$$

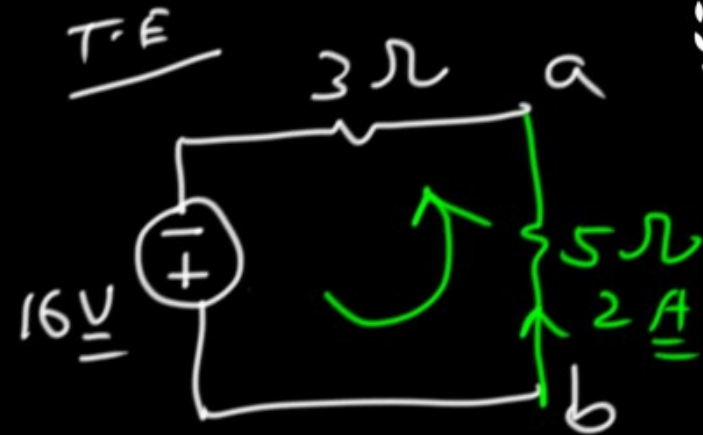


$$P_{abs} = (2)^2 (5)$$

$$= 20 \text{ W}$$

⑥ Norton

$$\underline{S-I} \quad R_N = R_{TH} = 3\Omega$$

$$\underline{S-II} \quad I_N$$

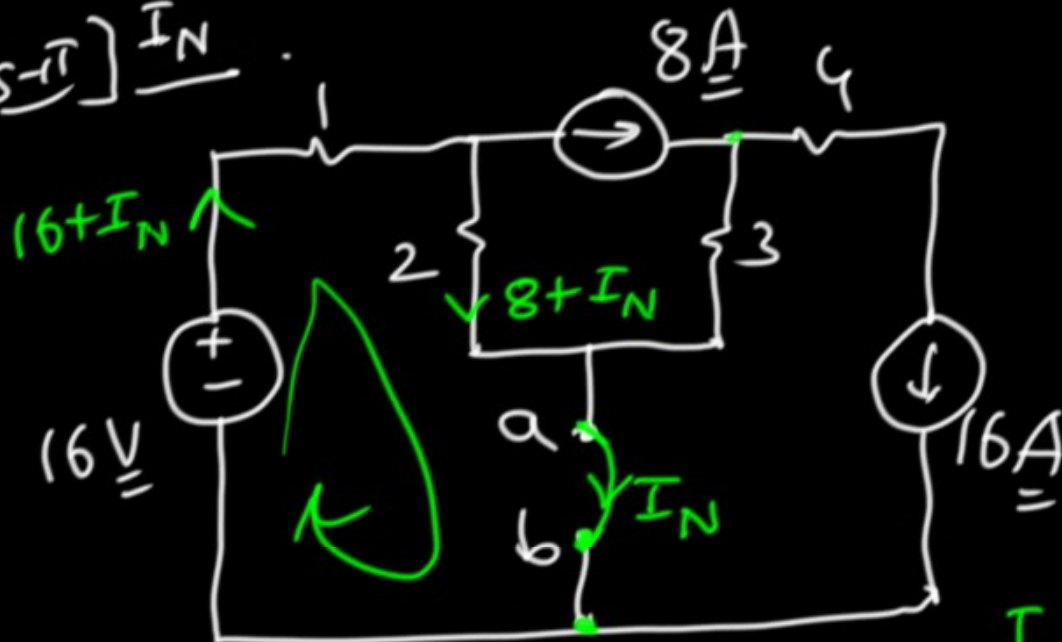

KCL + KVL

$$-16 + 1[16 + I_N]$$

$$+ 2[8 + I_N] = 0$$

$$I_N = -\frac{16}{3} A$$




$$I_{5\Omega} = \frac{16}{3} \times \frac{3}{8} = 2A \uparrow$$

$$P_{abs} = 2^2(5) = 20W$$


GATE/IM:

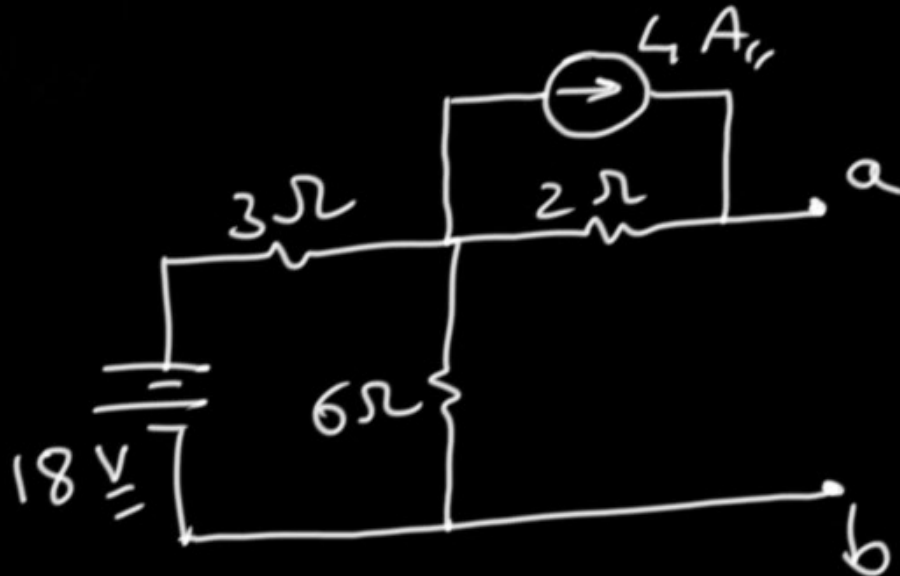Determine T.E & N.E across terminals a-b.




@ T.T

S-I }  $R_{TH} = R_{TH}$

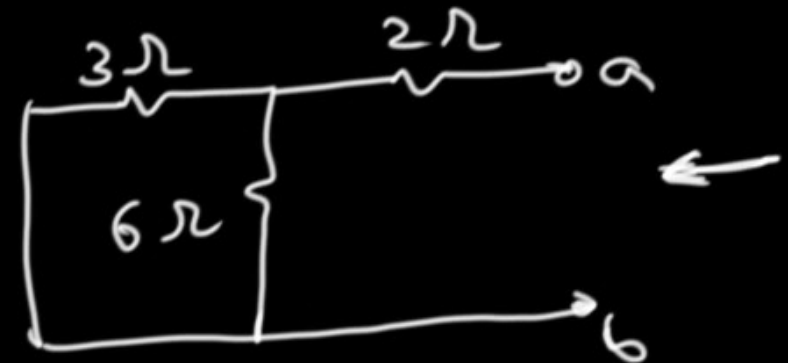


$= 4\Omega$

S-π]  $V_{TH}$ :

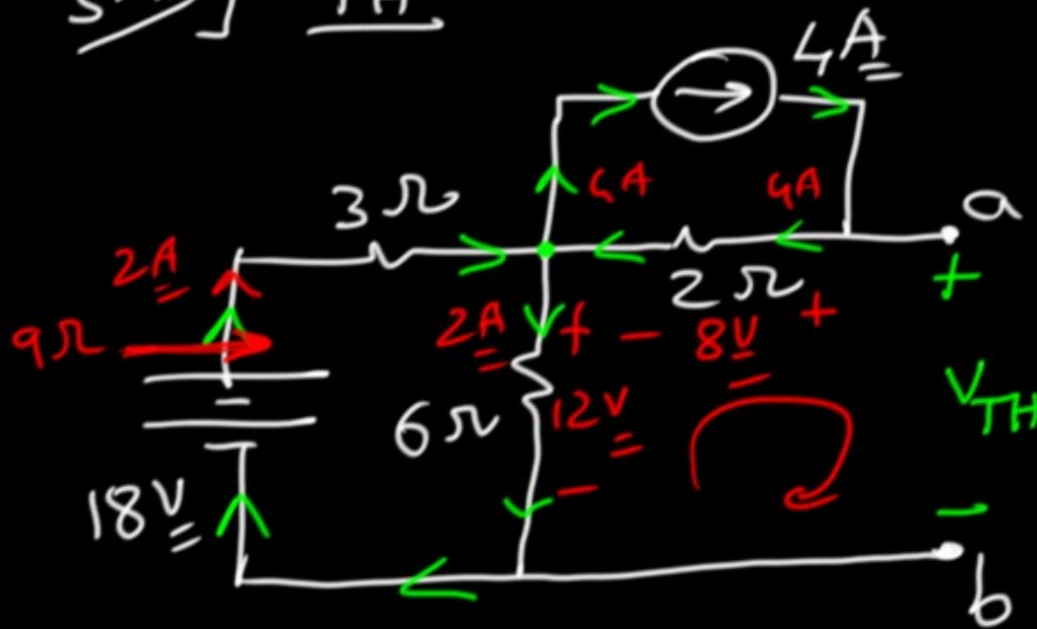



KVL  $-12 - 8 + V_{TH} = 0$


$V_{TH} = +20V$

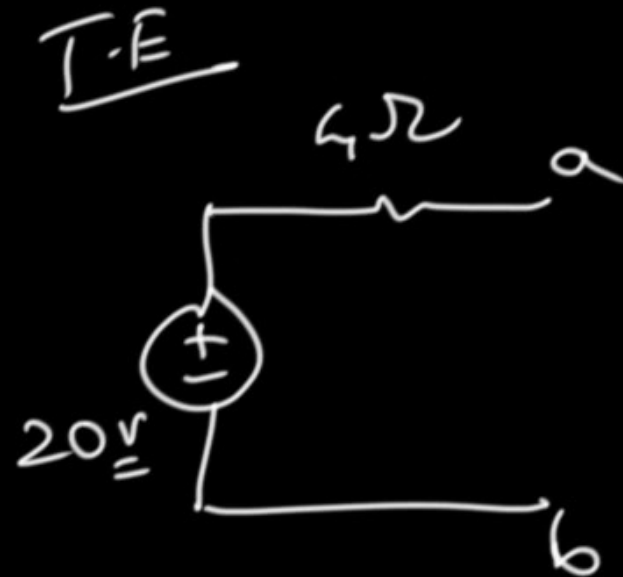

⑥ N.T  $S-I$   $R_N = R_{N+} = \underline{4\Omega}$

$S-I$   $\underline{I_N}$

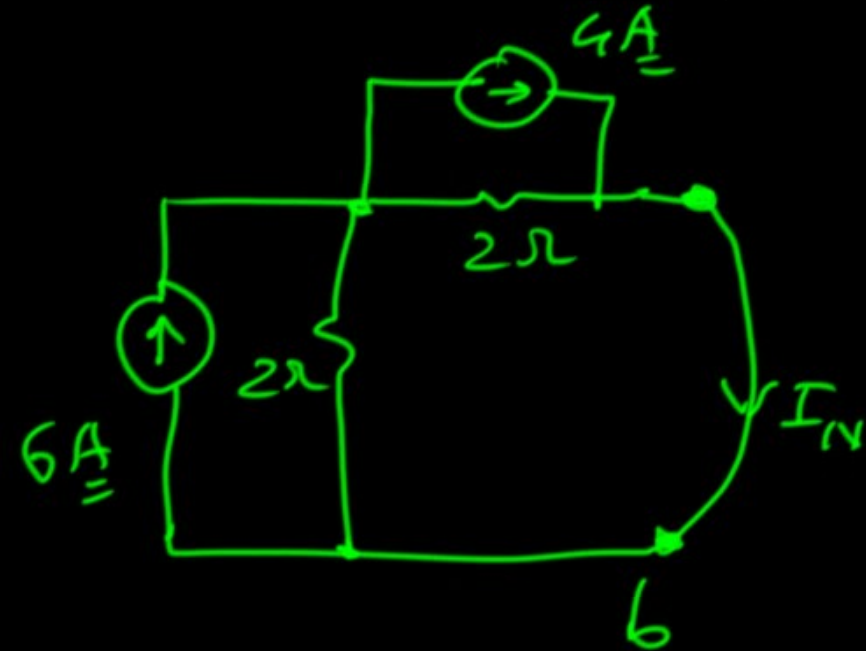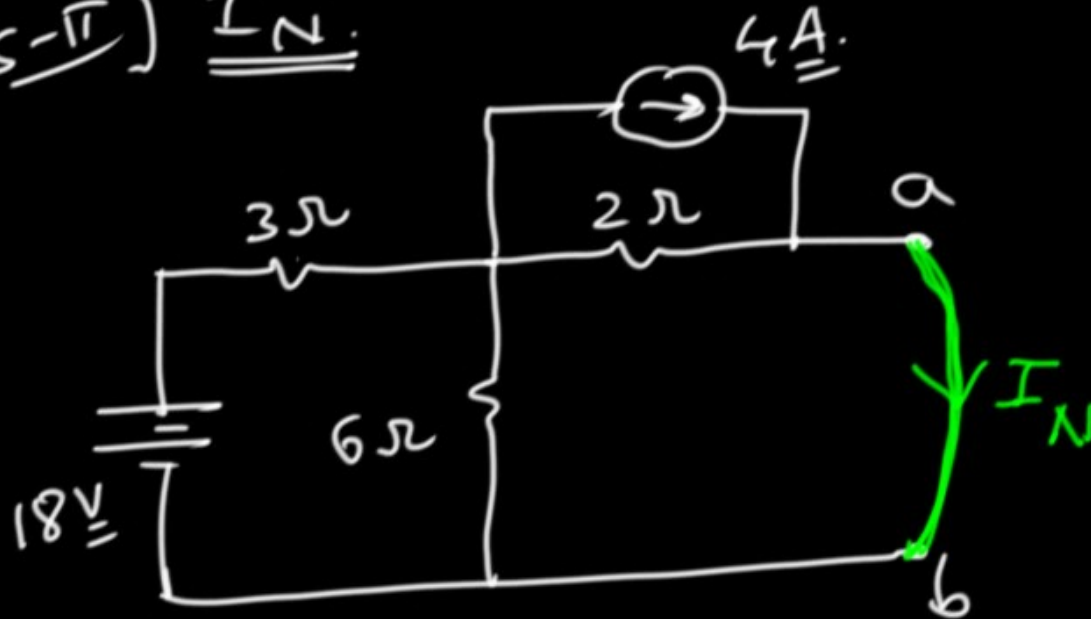


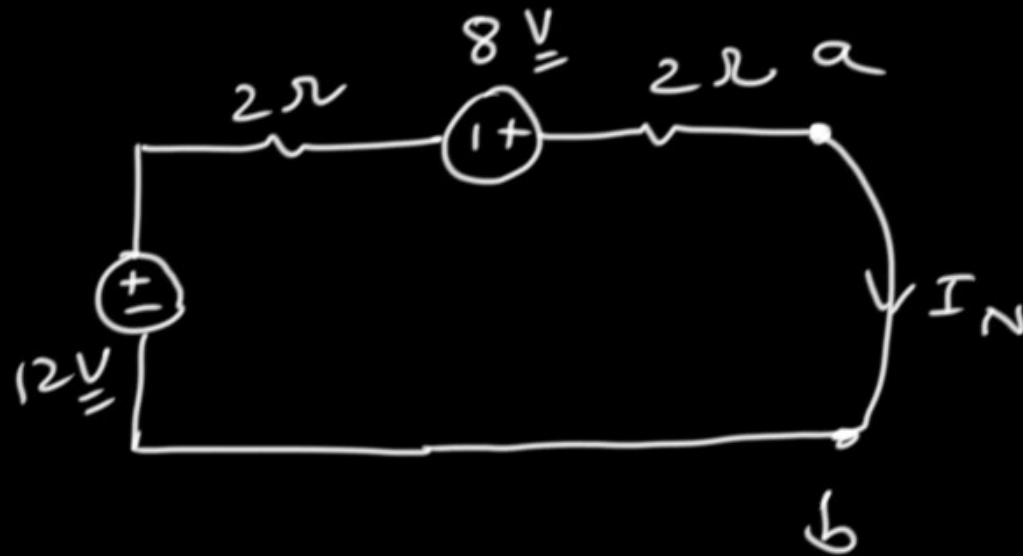

KVL

$$-12 + 2I_N - 8 + 2I_N = 0$$


$$I_N = \underline{\underline{5A}}$$

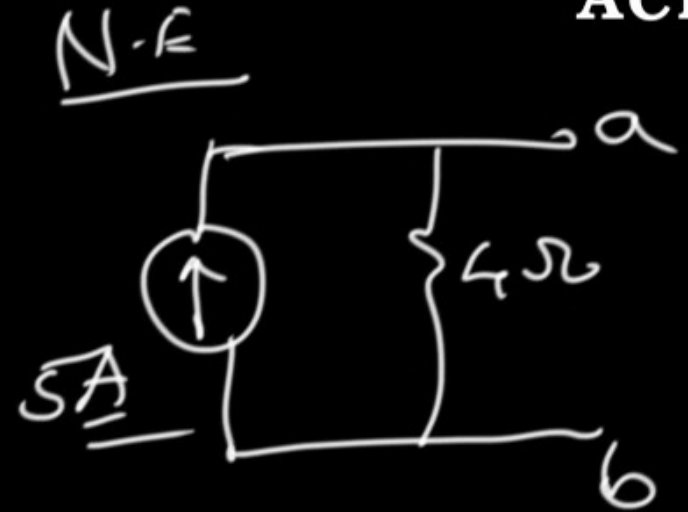




GATE/2M

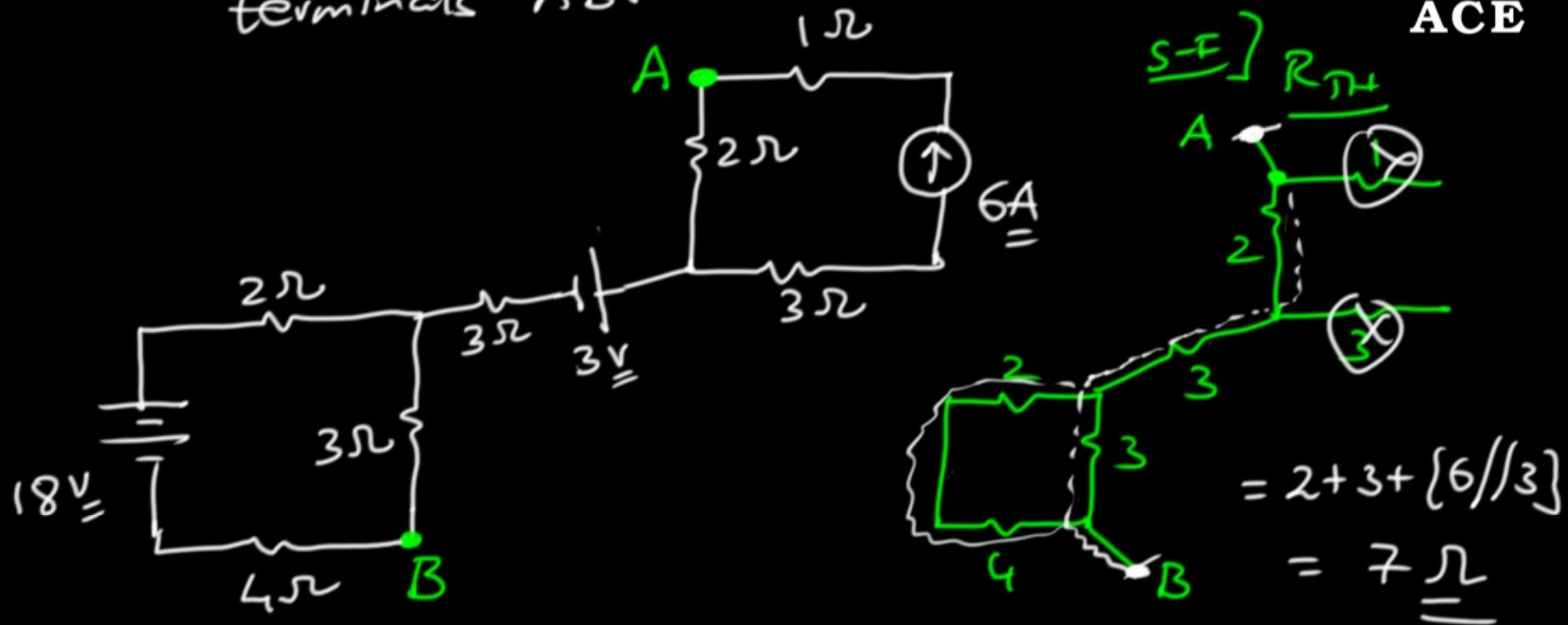Find Thevenin's equivalent across terminals AB.




5-17 ]  $V_{TH}$

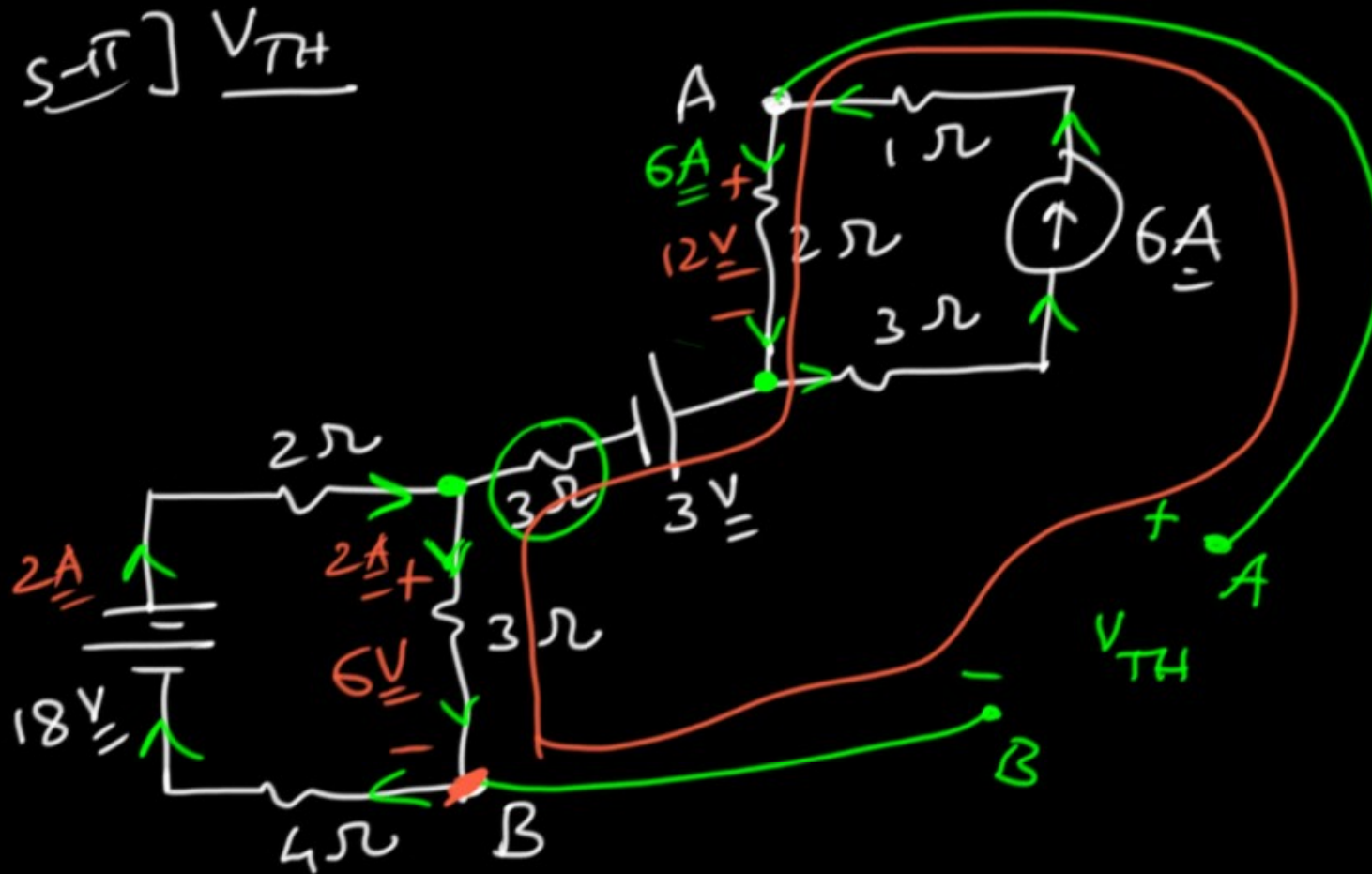


$$\frac{12V}{-6-3-12+V_{TH}} = 0$$

$$V_{TH} = +21V$$


T.F

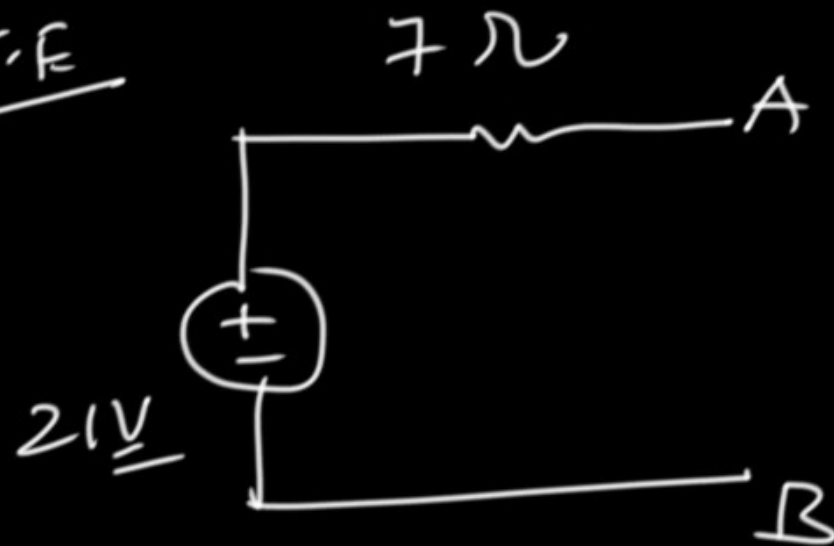

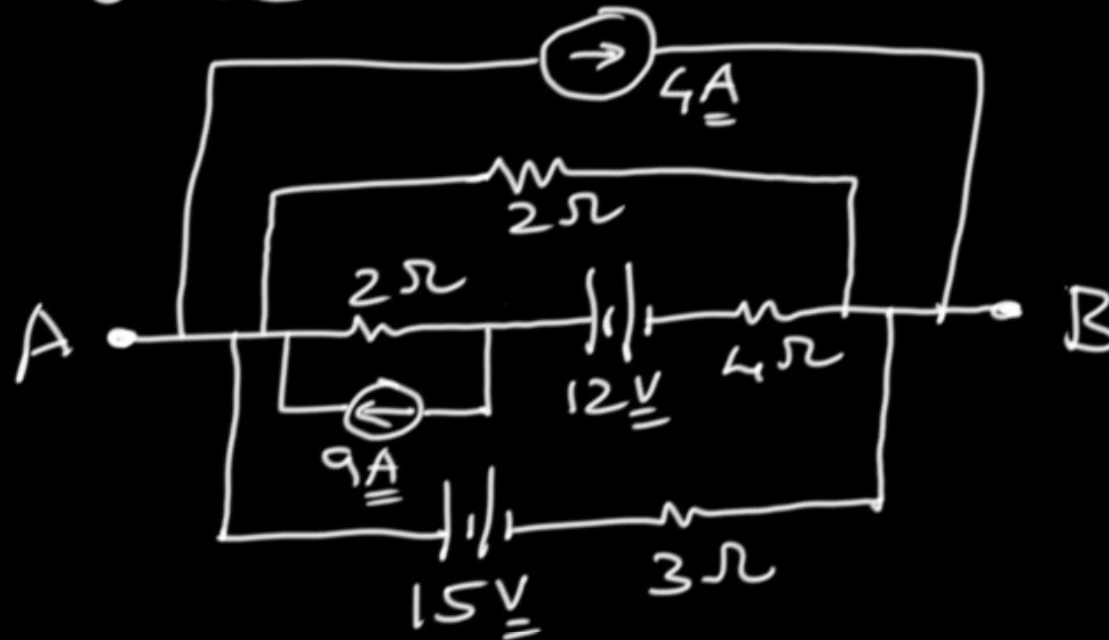Q] GATE/IM Determine Norton's Equivalent across terminals A-B.


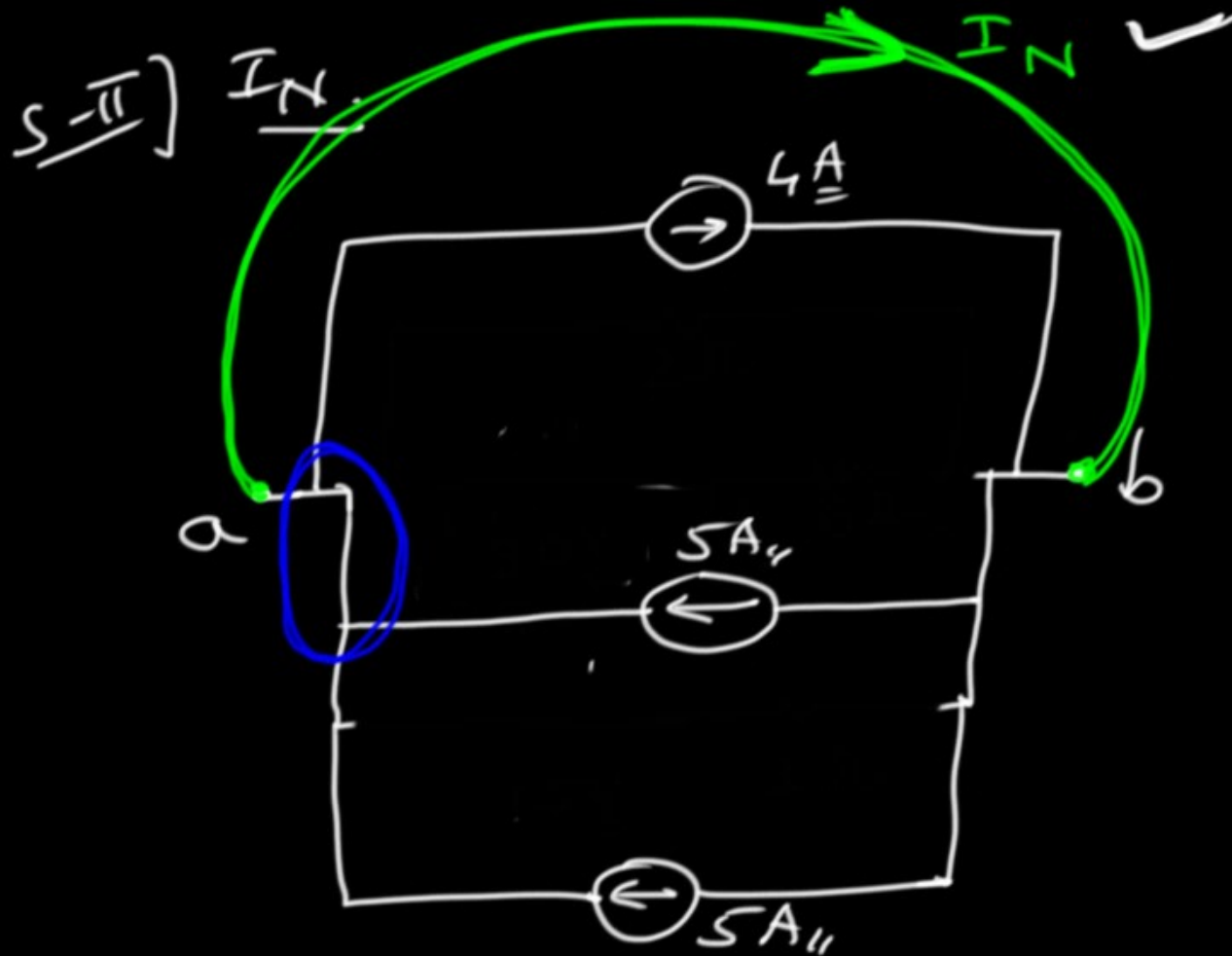
$$\begin{aligned} \text{S-F] } R_N &= 2 \parallel 6 \parallel 3 \\ &= \underline{\underline{1\Omega}} \end{aligned}$$




KCL


$$5 + 5 = 4 + I_N$$

$$I_N = \underline{\underline{6A}}$$


N-E

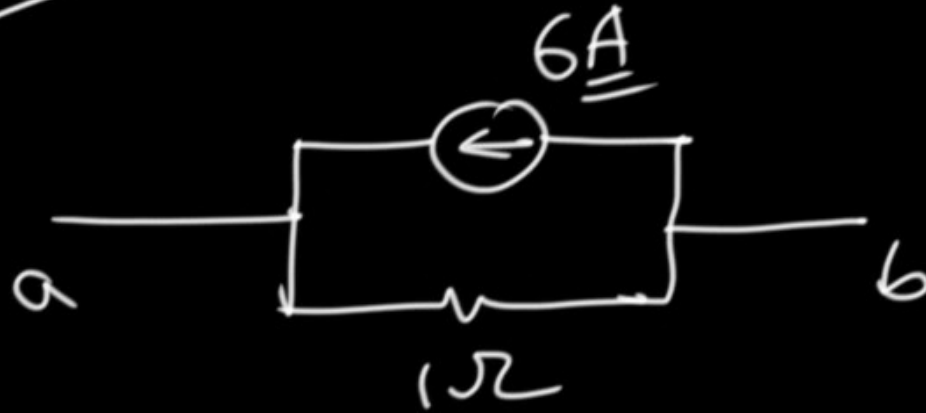


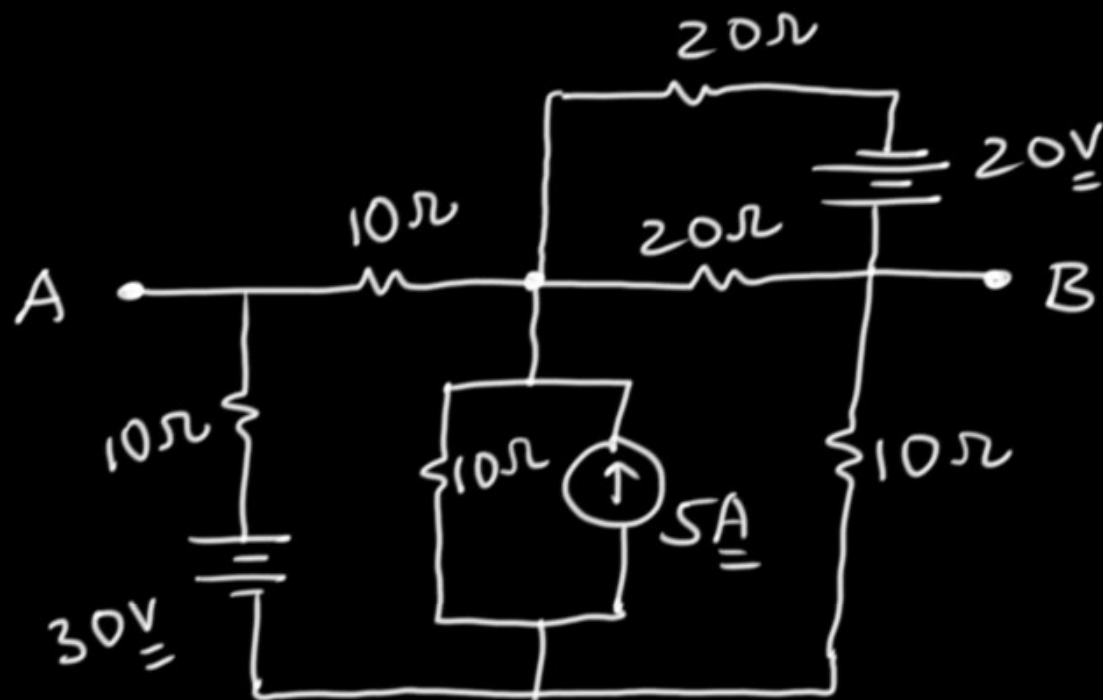IES [C] Determine Thevenin's & Norton's equivalent across A-B



S-I  $R_{TH} = R_N$

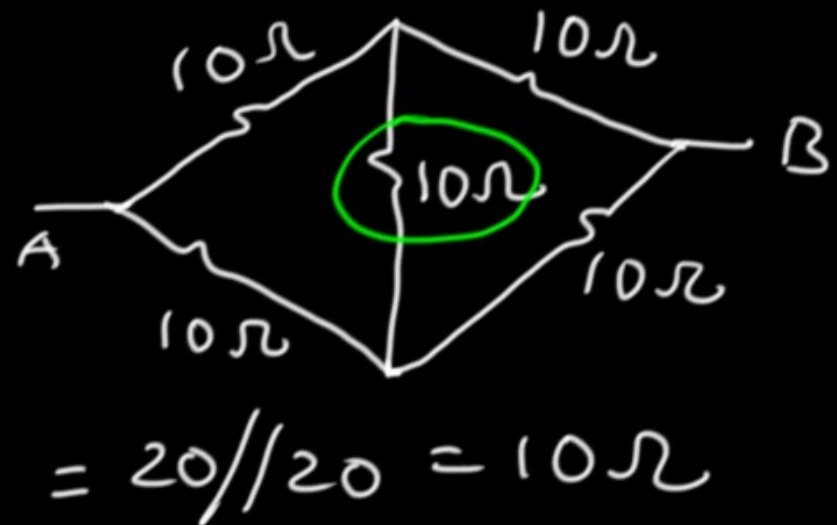

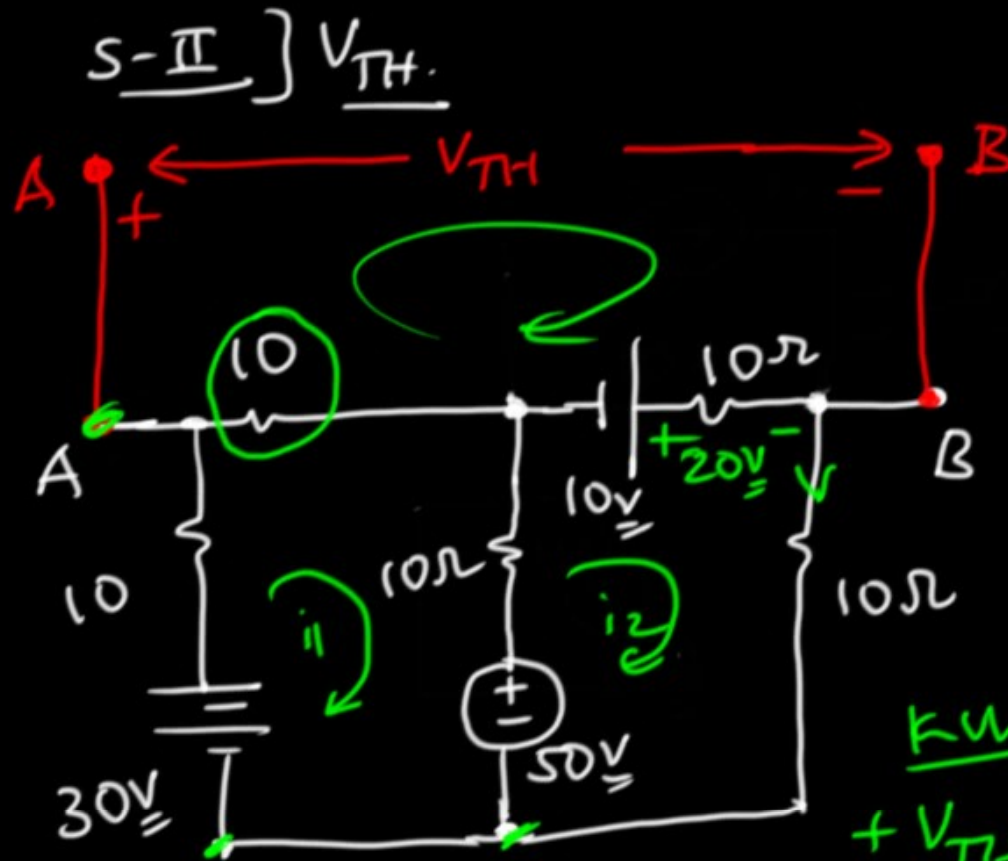

Mesh

$$-30 + 20i_1 + 10[i_1 - i_2] + 50 = 0$$

$$3i_1 - i_2 = -2 \quad \text{--- (1)}$$

$$-50 + 10[i_2 - i_1] - 10 + 20i_2 = 0$$

$$-i_1 + 3i_2 = 6 \quad \text{--- (2)}$$

$$8i_2 = 16 \rightarrow \boxed{i_2 = 2A}$$

$$\boxed{i_1 = 0A}$$


KVL


$$+V_{TH} - 20 + 10 = 0$$

$$\boxed{V_{TH} = +10 \text{ volts}}$$



T-E

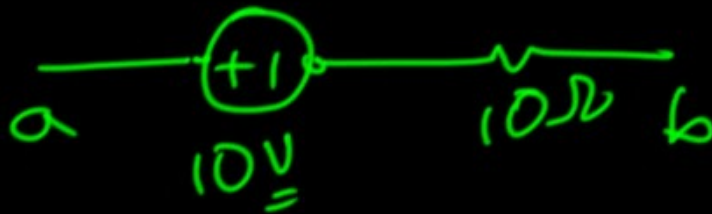

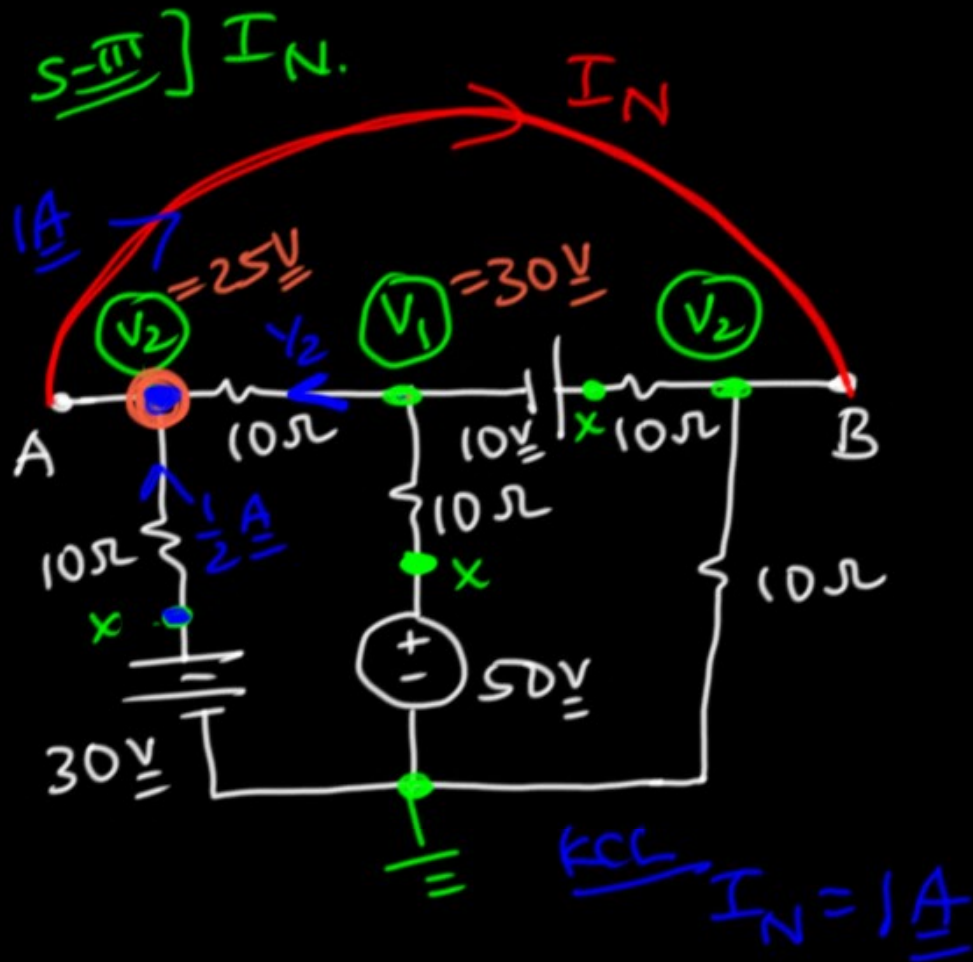

Nodal

$$\frac{(V_1 - V_2)}{10} + \frac{(V_1 - 50)}{10} + \frac{(V_1 - V_2 + 10)}{10} = 0$$


$$3V_1 - 2V_2 = 40 \quad \text{--- (1)}$$

$$\frac{(V_2 - V_1)}{10} + \frac{(V_2 - 30)}{10} + \frac{V_2}{10} + \frac{(V_2 - V_1 - 10)}{10} = 0$$

$$-2V_1 + 4V_2 = 40$$

$$-V_1 + 2V_2 = 20 \quad \text{--- (2)}$$
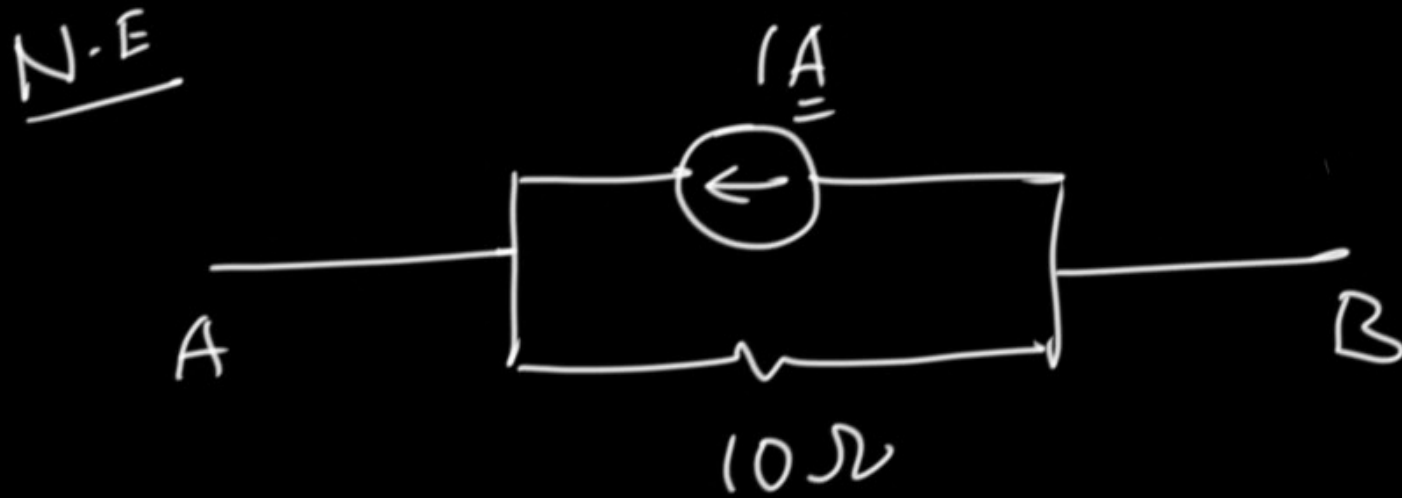
$$\boxed{V_1 = 30V}, \quad \boxed{V_2 = 25V}$$





Cat-II] Problems with both independent & dependent sources

→ In such networks determining  $R_{TH}$  (or)  $R_N$  is not possible directly due to the presence of dependent sources, moreover the N/w is already active & working due to the presence of independent source in it. In such N/w's we use OHM's Law to indirectly find resistance, where

$$R_{TH} = R_N = V_{OC} / I_{SC} \quad \text{at the target terminals}$$

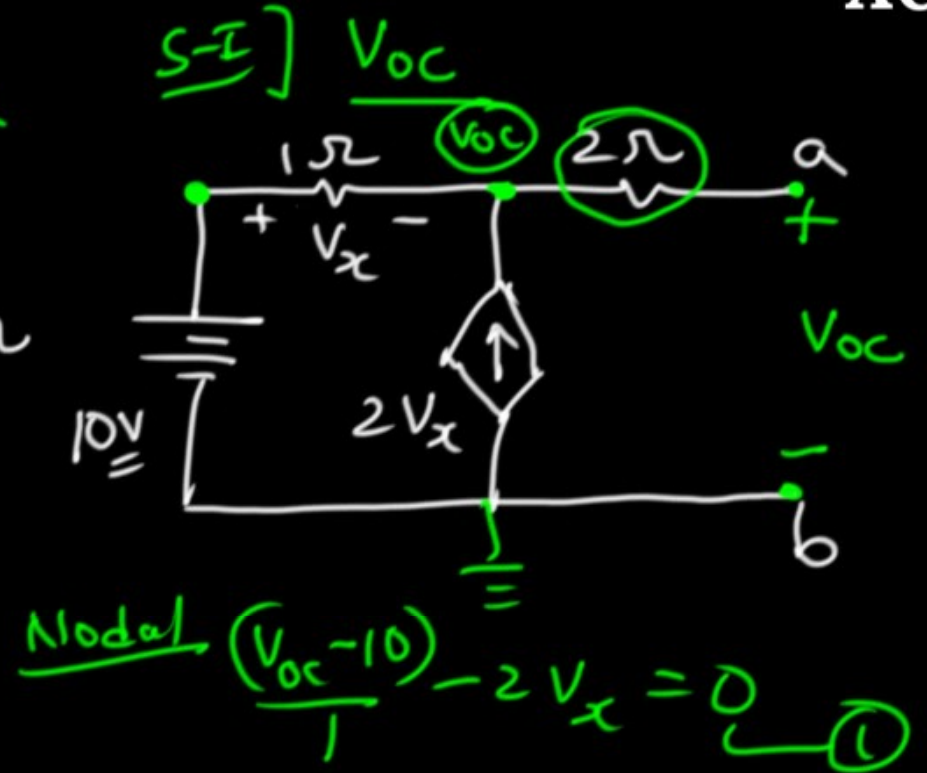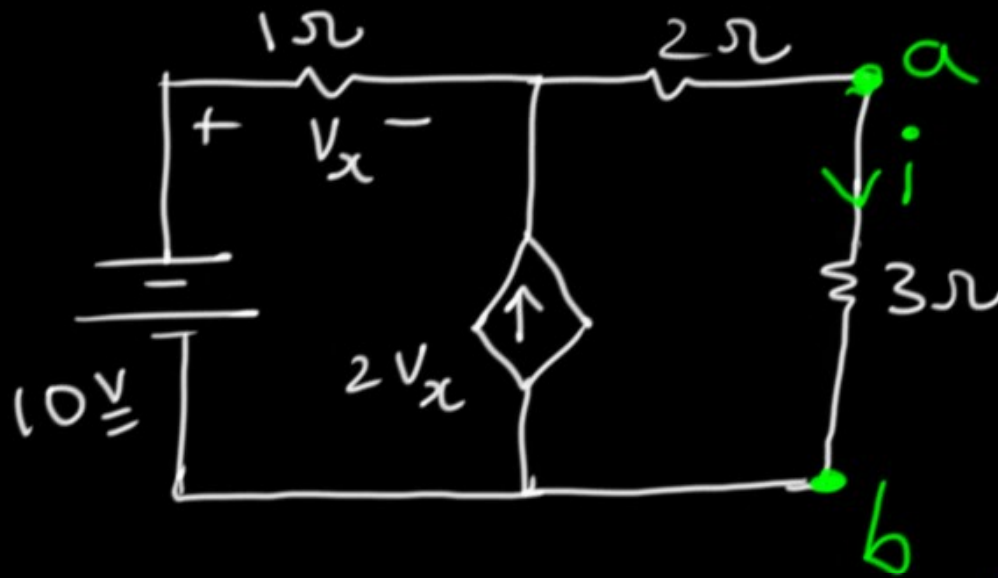① Find Current 'i' in the circuit by using Thevenin's & Norton's Theorem




$$V_x = 10 - V_{oc} \quad \text{--- (2)}$$

$$V_{oc} - 10 - 20 + 2V_{oc} = 0$$

$$3V_{oc} = 30$$

$$\boxed{V_{oc} = 10 \text{ V}}$$

S-II]  $I_{sc}$

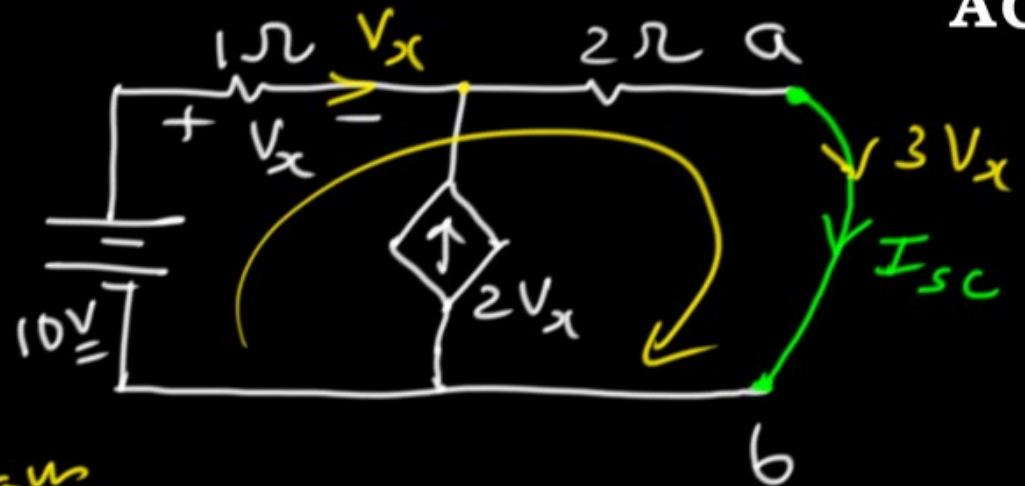



KVL

$$-10 + V_x + 2[3V_x] = 0 \rightarrow V_x = \frac{10}{7} \text{ V}$$

Then  $I_{sc} = 3V_x = \frac{30}{7} \text{ A}$

Now

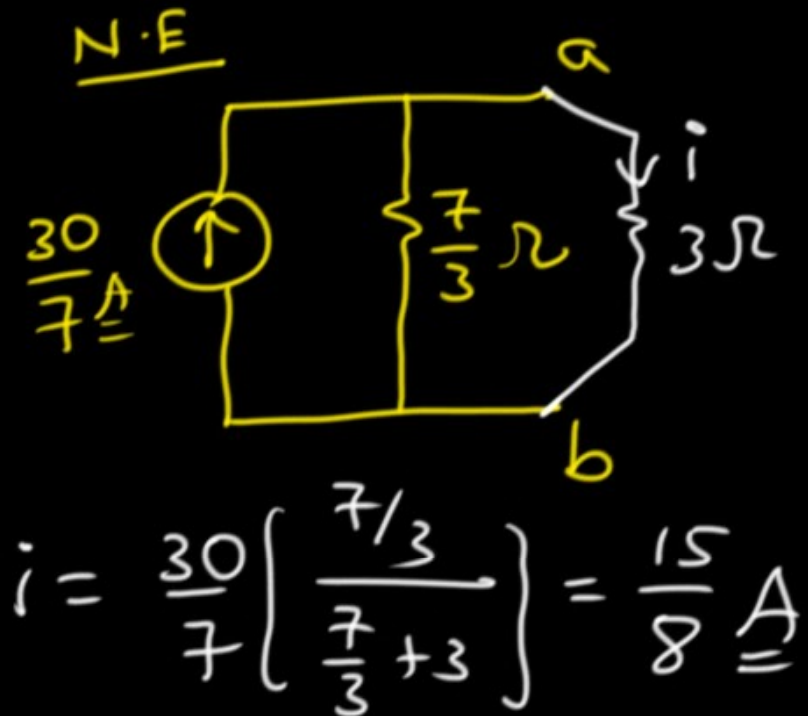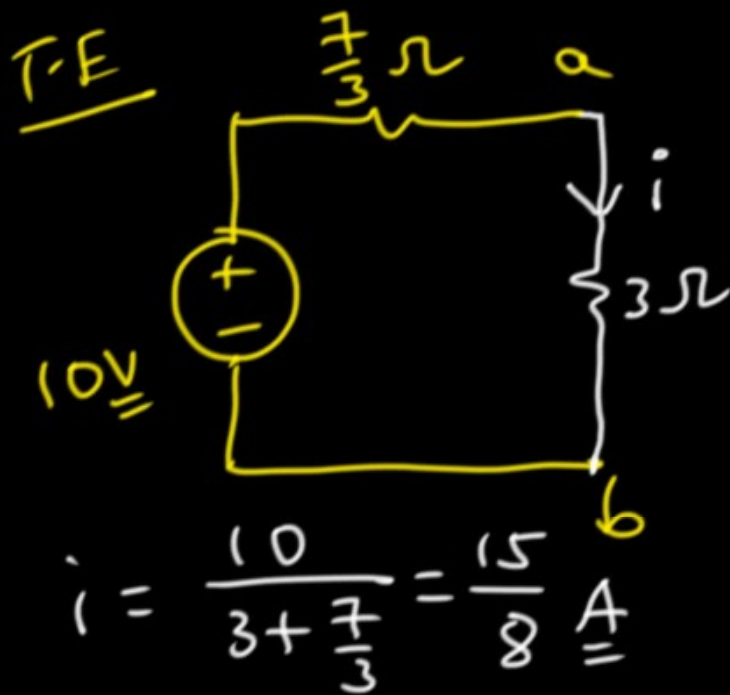
$$R_{TH} = R_N = \frac{V_{OC}}{I_{SC}} = \frac{10}{30/7} = \frac{7}{3} \Omega$$






Note: In this category -II problems sometimes if it is required only to find resistance but not equivalent then de-activate N/w & apply Ohm's Law directly.

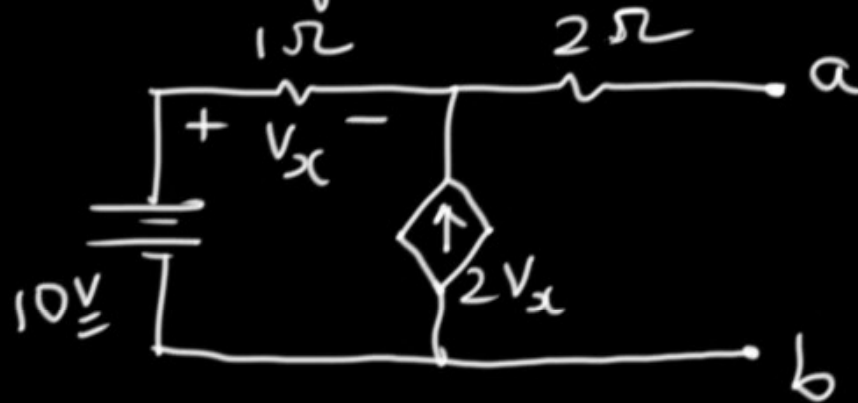→ Modify previous (9) only to find  $R_{TH}/R_N$





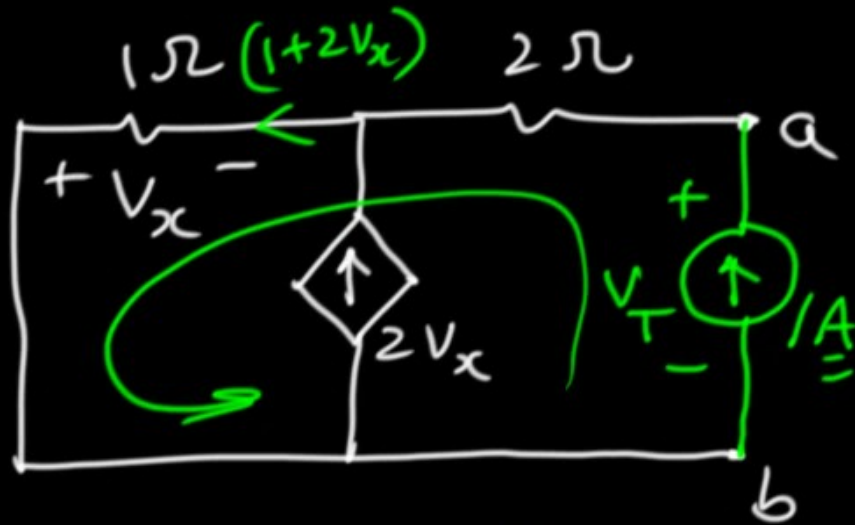

KVL  $-V_T + 2 + 1[1 + 2V_x] = 0$

$V_T = 3 + 2V_x$  (1)

Link

$V_x = -1[1 + 2V_x]$


$3V_x = -1$  (2)

$V_T = 3 + 2\left[-\frac{1}{3}\right]$


$V_T = \frac{7}{3} \text{ volt}$

$R_{Th} = R_N = \frac{V_T}{1} = \frac{7}{3} \Omega$

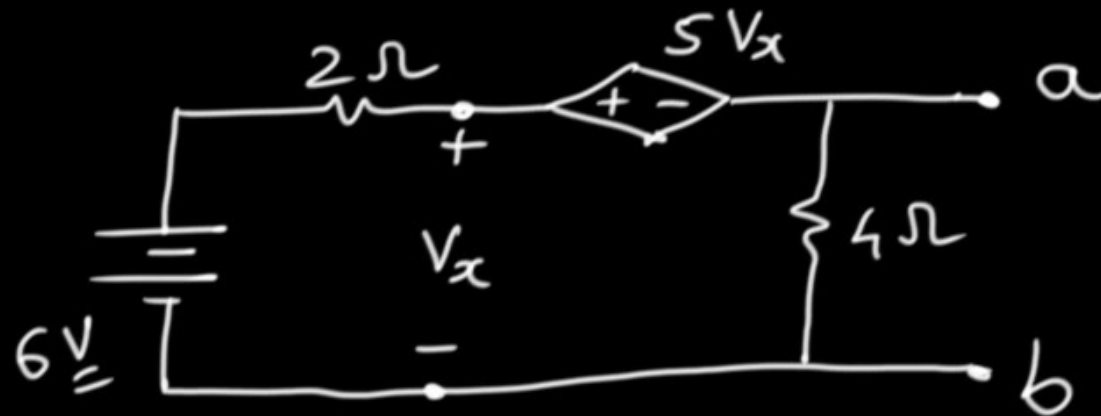GATE/2M Determine Norton's equivalent  
between a-b.



S-I  $V_{oc}$

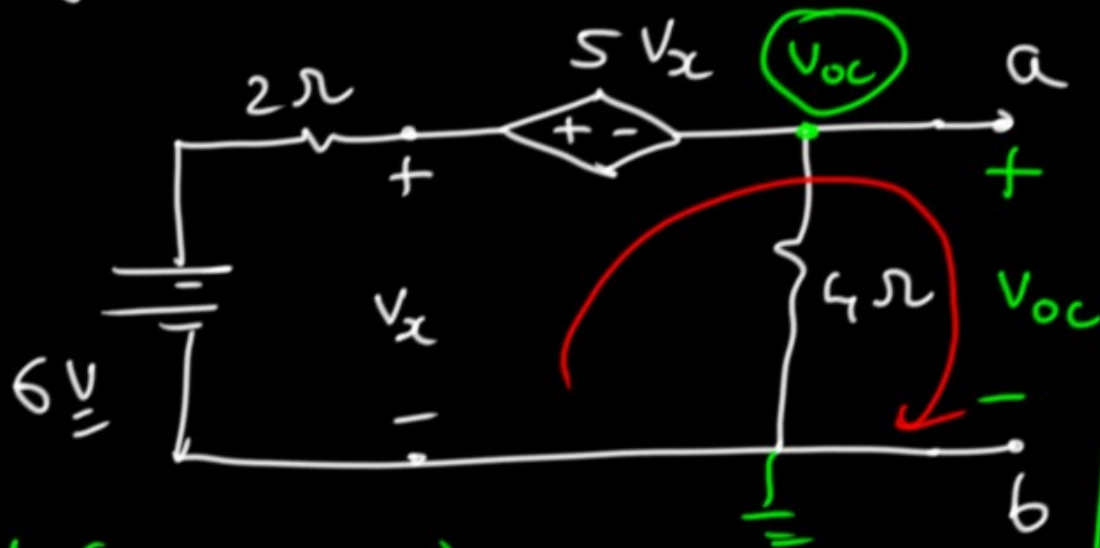

KVL

$$-V_x + 5V_x + V_{oc} = 0$$

$$V_{oc} = -4V_x \quad (2)$$


$$3V_{oc} + 10 \left[ \frac{-V_{oc}}{4} \right] = 12$$

$$\boxed{V_{oc} = 24} \text{ V}$$

Nodal  $\frac{(V_{oc} - 6 + 5V_x)}{2} + \frac{V_{oc}}{4} = 0$

$$3V_{oc} + 10V_x = 12 \quad (1)$$
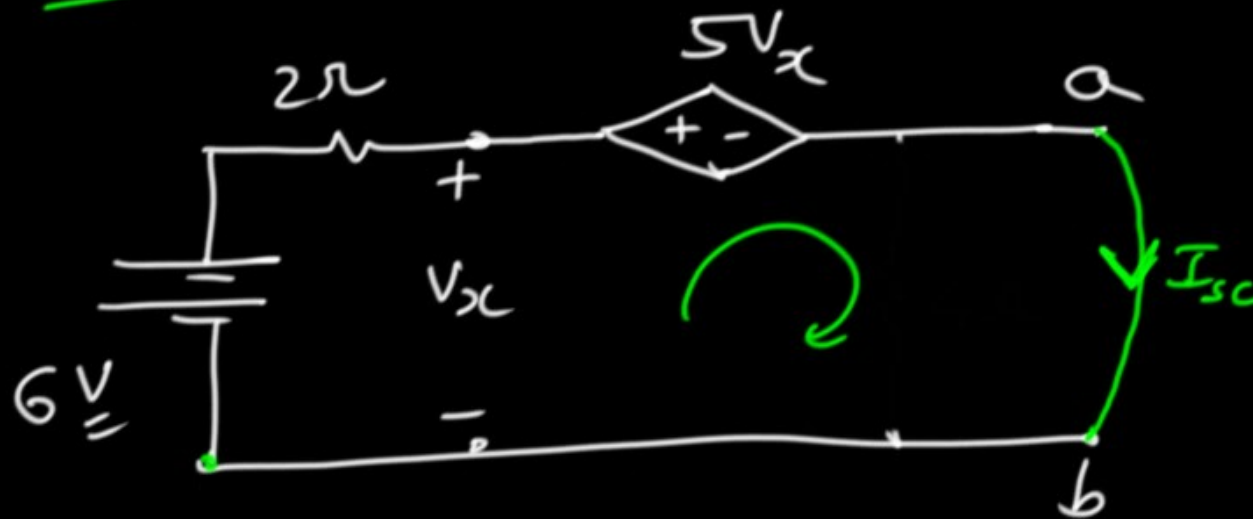
$$\underline{5 - \pi} \} \underline{I_{sc}}$$



Mesh  $-6 + 2I_{sc} + 5V_x = 0$  (1)


CVS  $-V_x + 5V_x = 0 \rightarrow V_x = 0$  (2)

$$2I_{sc} = 6$$

$$\underline{I_{sc} = 3 \text{ A}}$$

$$R_N = \frac{V_{oc}}{I_{sc}} = \frac{24}{3} = 8\Omega$$


N.E

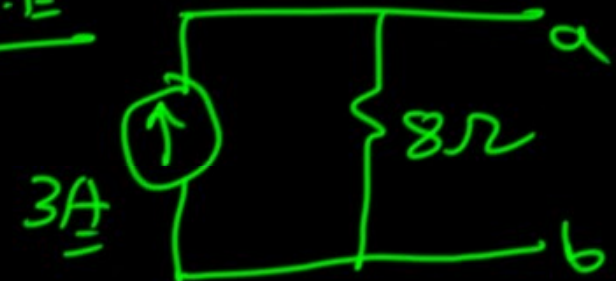

GATE/2M

Determine Thevenin's equivalent  
across the Load.

S-F)  $V_{oc}$

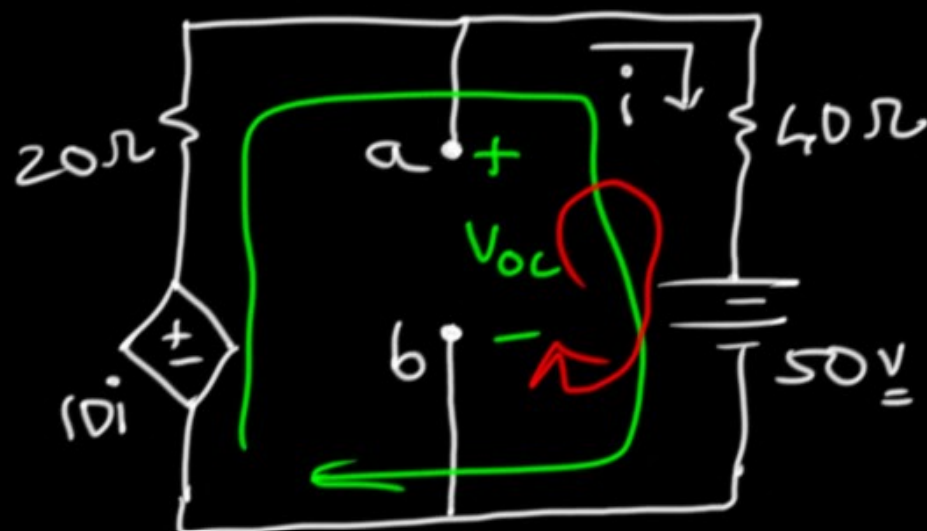

Math  $-10i + 20i + 40i + 50 = 0$   
 $i = -1 \text{ A}$  — (1)

KVL

$$-V_{oc} + 40i + 50 = 0$$


$$V_{oc} = 50 + 40i$$

$$V_{oc} = 50 + 40(-1)$$


$$V_{oc} = 10 \underline{\underline{V}}$$


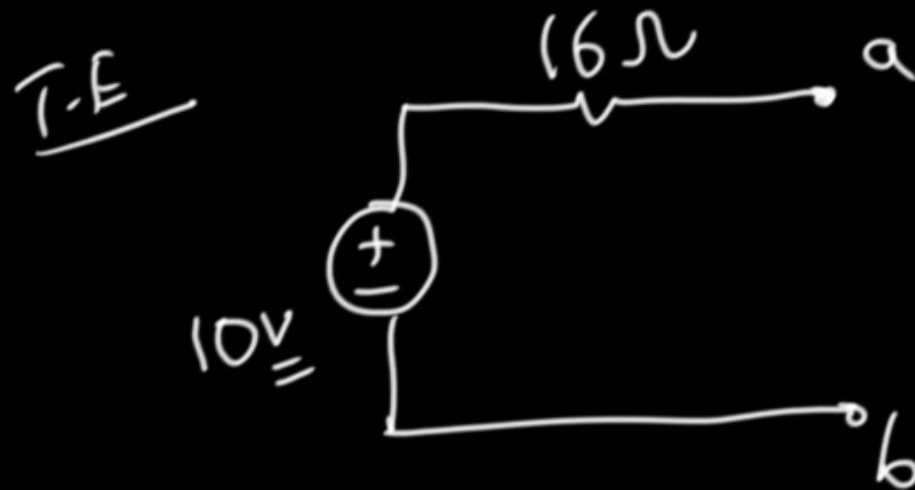
$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{10}{5/8} = \underline{\underline{16\Omega}}$$




GATE/IM

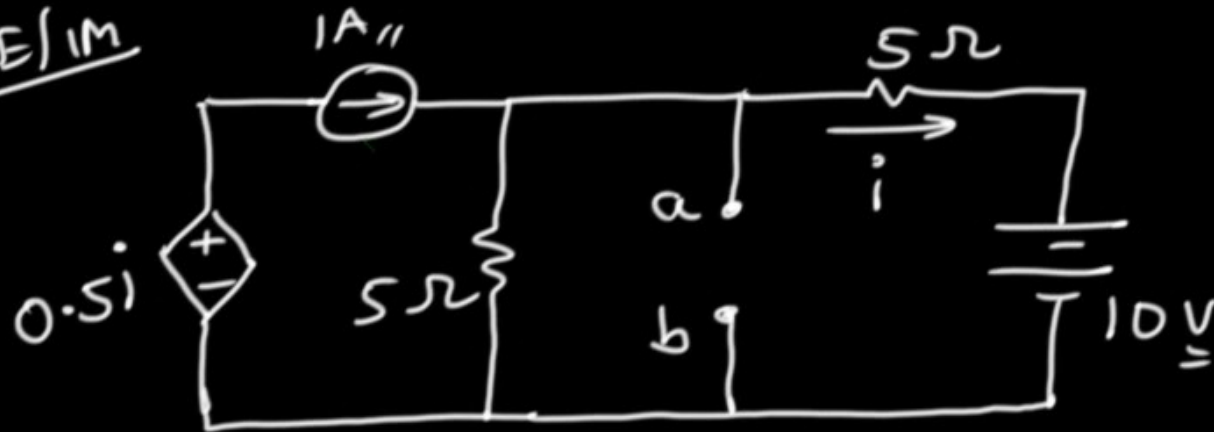

The Thevenins resistance across terminals a-b  $5\Omega$  is —

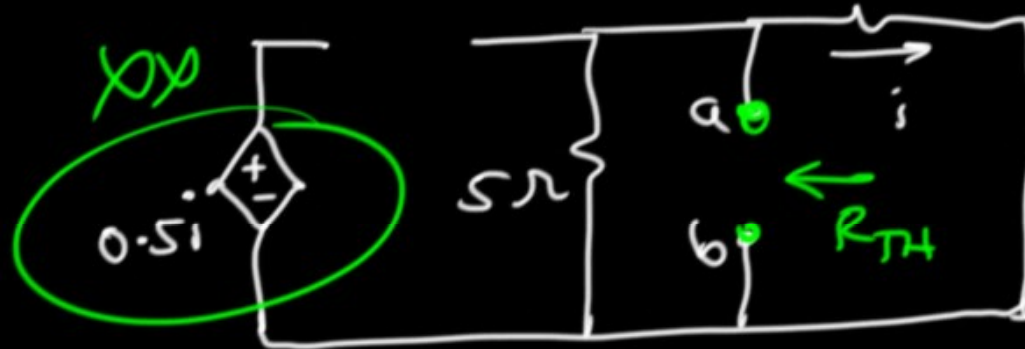- a)  $0\Omega$
- b)  $2.5\Omega$
- c)  $5\Omega$
- d)  $7.5\Omega$





so  
 $R_{TH} = 5 // 5$   
 $= \underline{\underline{2.5\Omega}}$




Application → special.

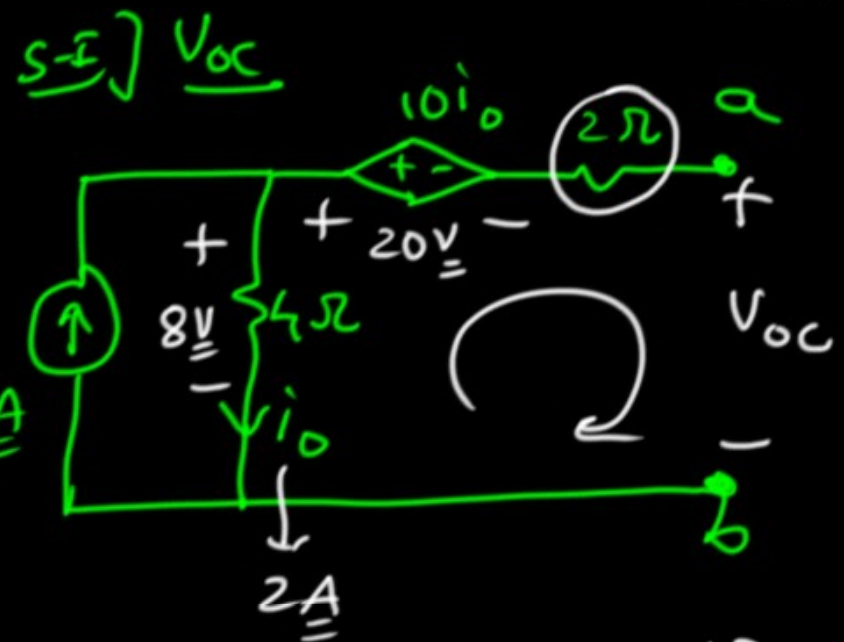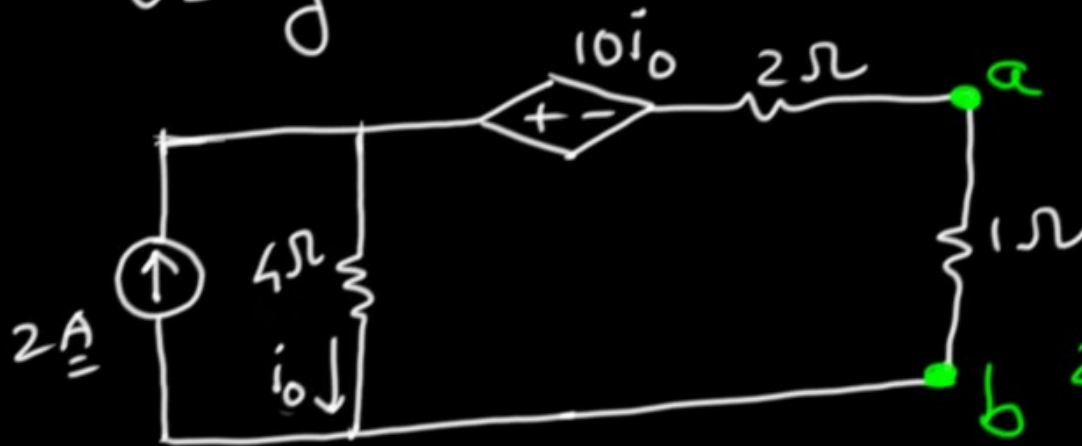Q] Determine current through  $1\Omega$  resistance using Norton's Theorem.



KVL  $-8 + 20 + V_{oc} = 0 \rightarrow V_{oc} = -12 \text{ volts}$

S-II }  $I_{sc}$

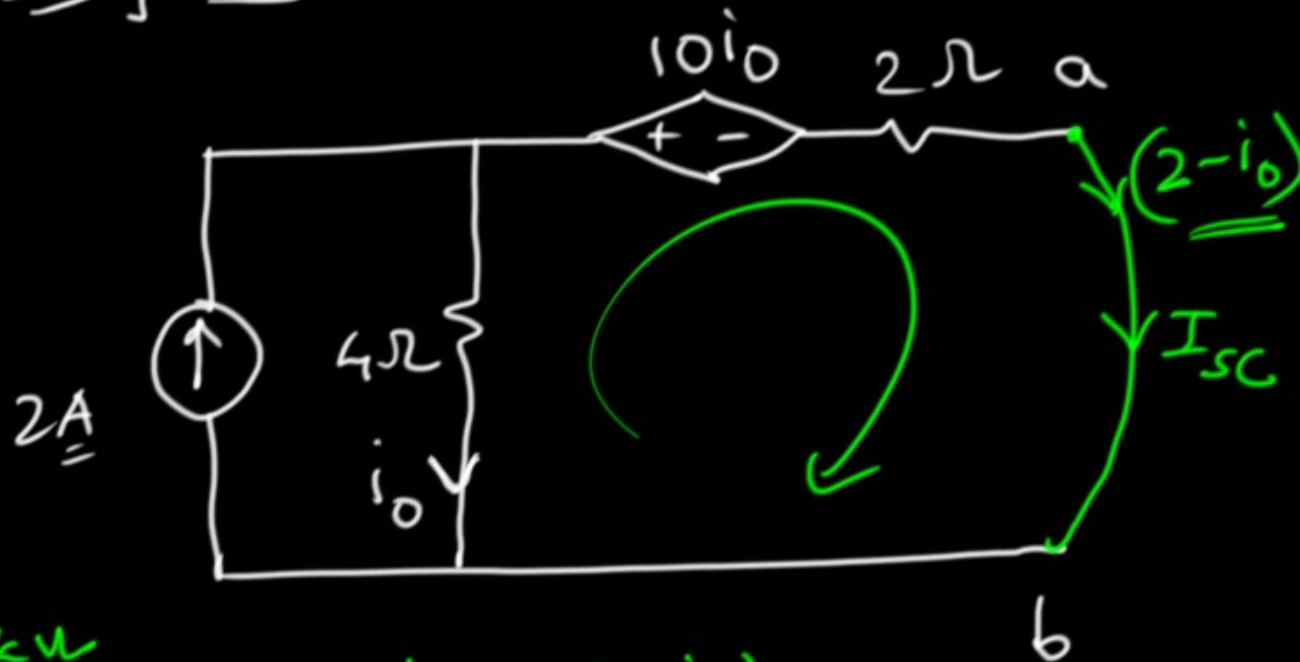

KVL

$$-4i_o + 10i_o + 2(2 - i_o) = 0$$

$$\underline{i_o = -1}$$


But

$$I_{sc} = 2 - i_o$$

$$I_{sc} = 2 - (-1)$$

$$= +3 \underline{A}$$

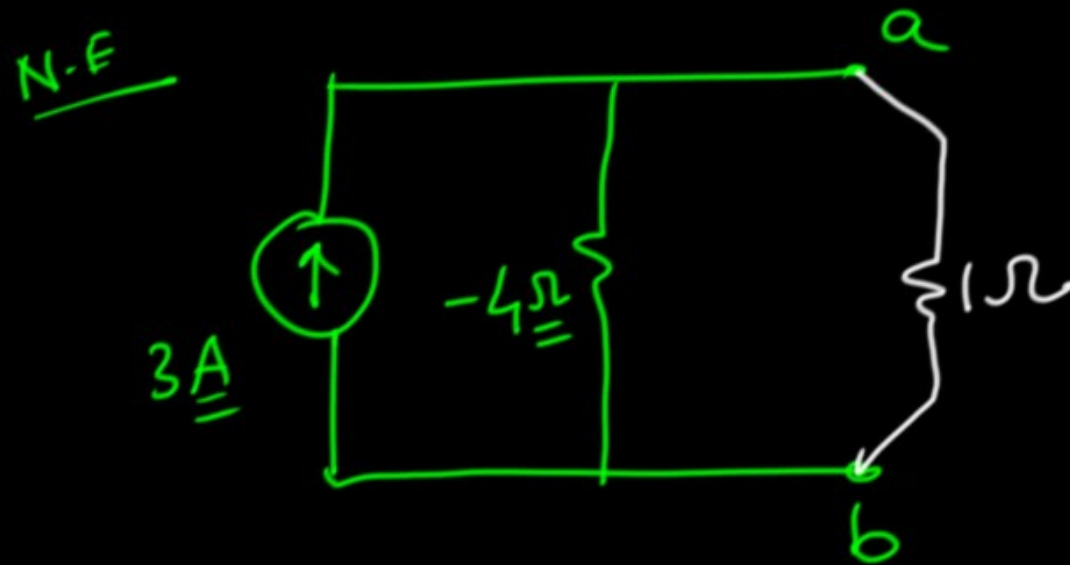
$$R_N = \frac{V_{oc}}{I_{sc}} = \frac{-12}{+3} = -\underline{\underline{4\Omega}} \quad \checkmark \checkmark$$



$$I_{1\Omega} = 3 \left[ \frac{-4}{-4+1} \right]$$

$$I_{1\Omega} = \underline{\underline{4A}}$$

Check directly

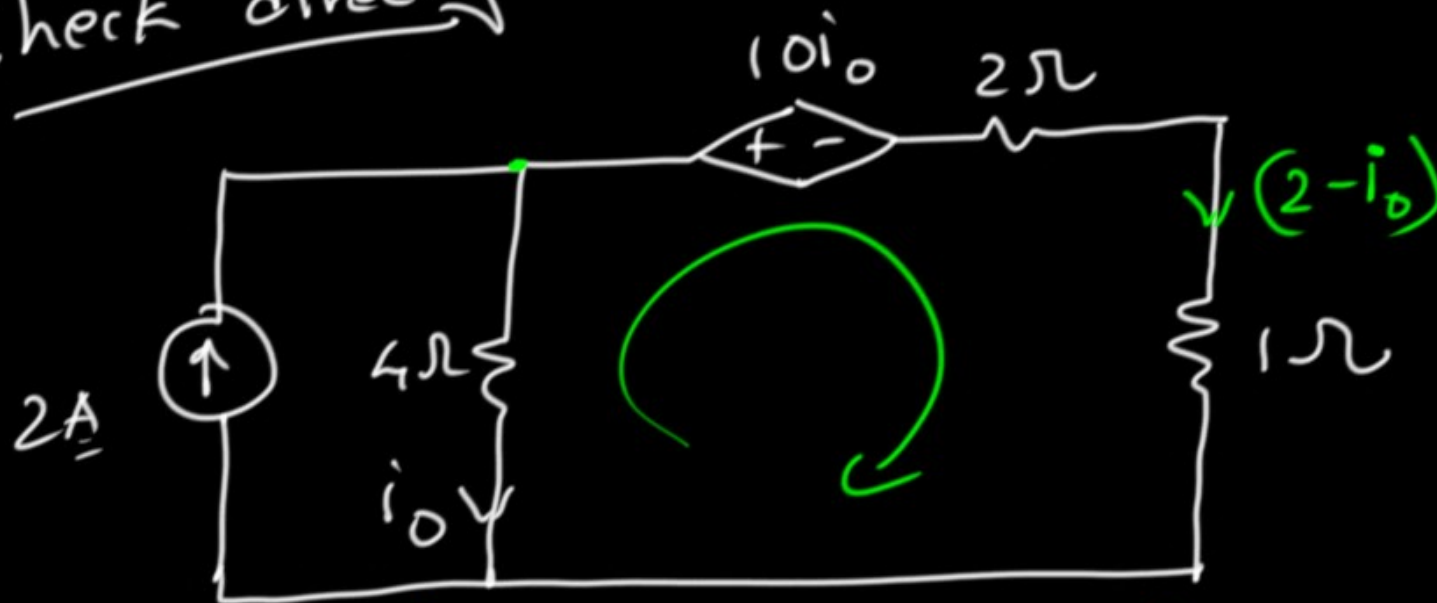


$$-4i_0 + 10i_0 + 3[2 - i_0] = 0 \quad \Bigg| \quad I_{1\Omega} = 2 - i_0 = 2 - (-2) = \underline{\underline{+4A}}$$


$$\underline{\underline{i_0 = -2A}}$$

Note: In the above problem  $R_N$  (or)  $R_{TH}$  is  $-ve$ ,  $(-ve)$  resistance is a characteristic way to model active regenerative N/w in electrical engineering whose operating  $V-i$  characteristic appears in Q-II (or) Q-IV  
Ex: High gain amplifiers, photo transistors  
solar cells, +ve feedback networks [oscillator]

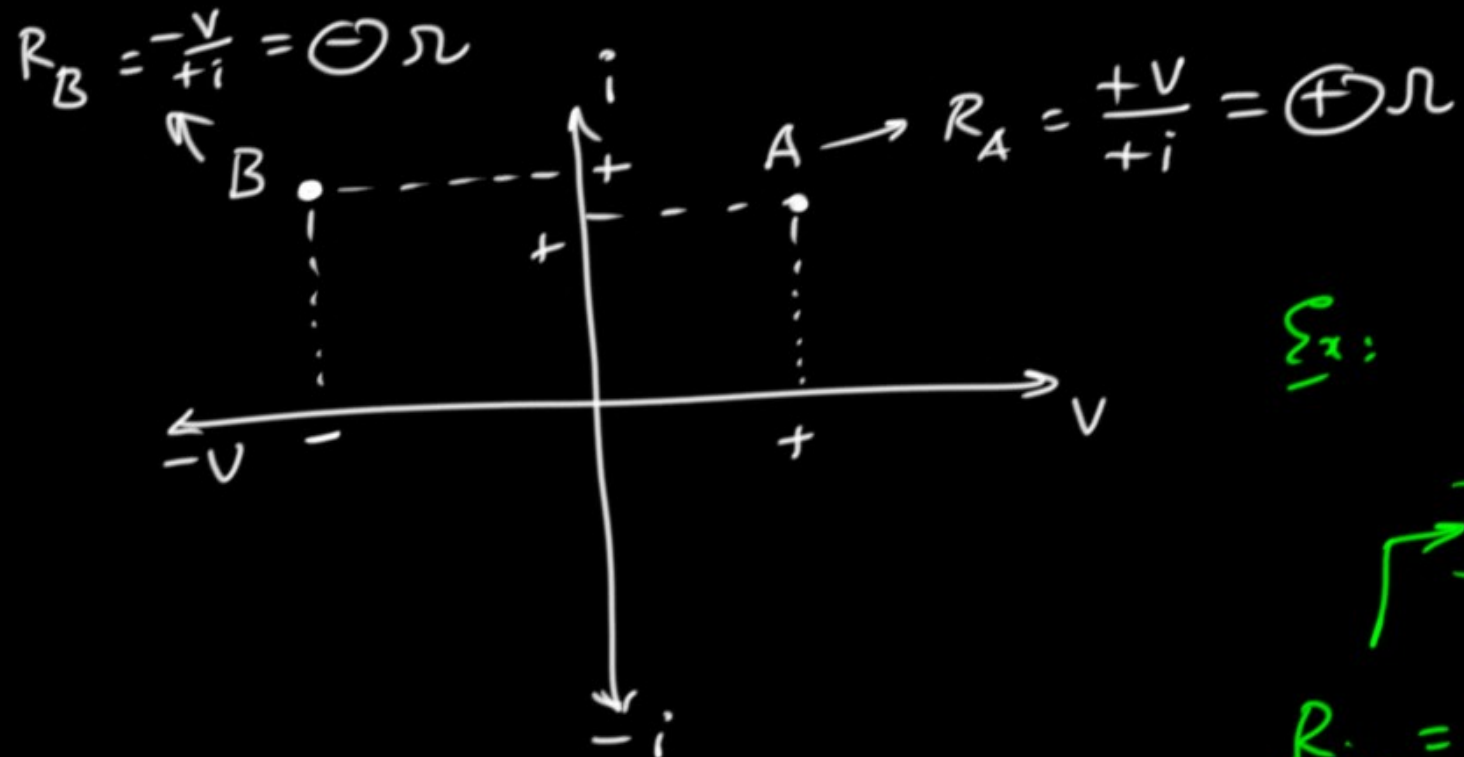Note: However,  $(-ve)$  Resistance is not a physically realizable quantity.



$\Sigma x$ :

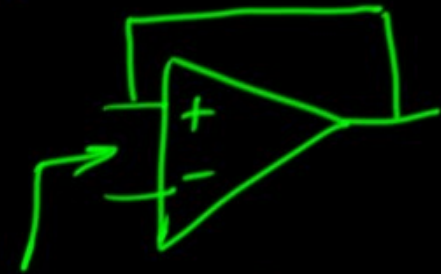

$R_{in} = (-V_o)$

## (Cat-III) Problems with only dependent sources

→ Such networks cannot work on their own, as there is no independent active element to drive them. In such N/w's ( $V_{TH} = 0V$ ) & ( $I_N = 0A$ ), however they have resistance. This resistance can be indirectly determined by Ohm's Law by externally exciting them, where


$$R_{TH} = R_N = \frac{1 \text{ volt}}{i_T} = \frac{V_T}{1 \text{ amp}}$$






GATE

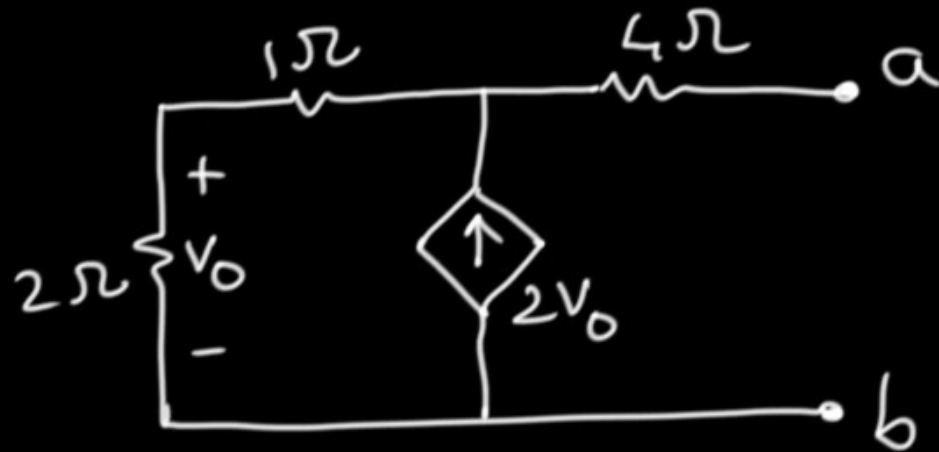Find Thevenin's & Norton's equivalent  
across terminals a-b.



$$\begin{array}{l} V_{TH} = 0 \text{ volts} \\ I_N = 0 \text{ Amps} \end{array} \quad \left| \quad \text{find 'R}_{TH}' \text{ by Ohm's Law} \right.$$

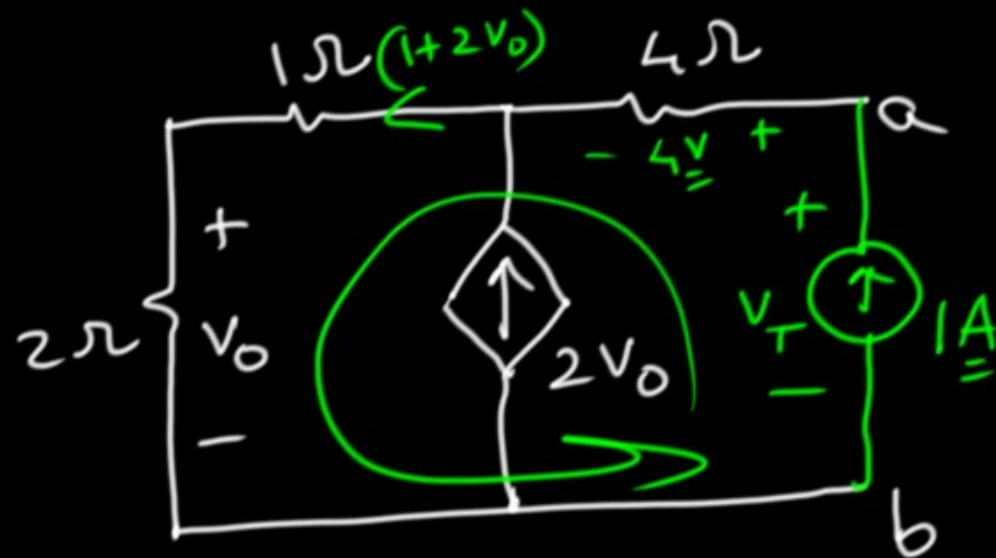

KVL

$$-V_T + 4 + 3[1 + 2V_0] = 0$$

$$V_T = (7 + 6V_0) \quad \text{--- (1)}$$

$$V_0 = 2[1 + 2V_0] \Rightarrow 3V_0 = -2 \quad \text{--- (2)}$$

$$V_T = 7 + 6\left[-\frac{2}{3}\right]$$

$$\underline{\underline{V_T = 3}}$$



$$R_{TH} = R_N = \frac{V_T}{I} = \underline{\underline{3 \Omega}}$$

T-E (or) N.E



ISRO

Thevenin's equivalent across a-b

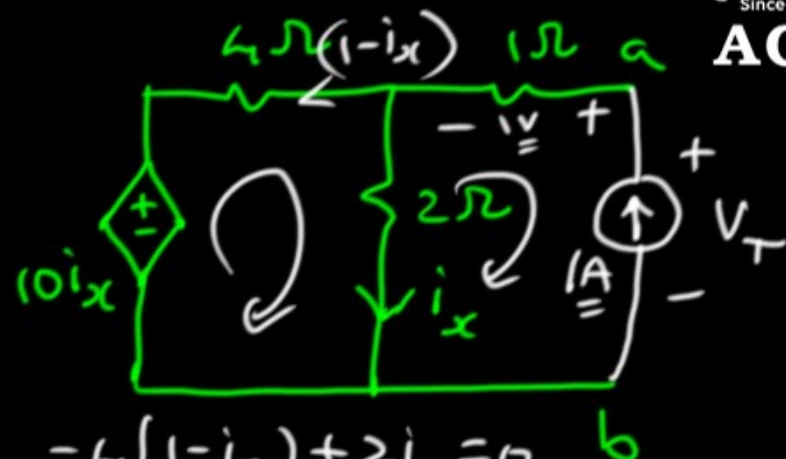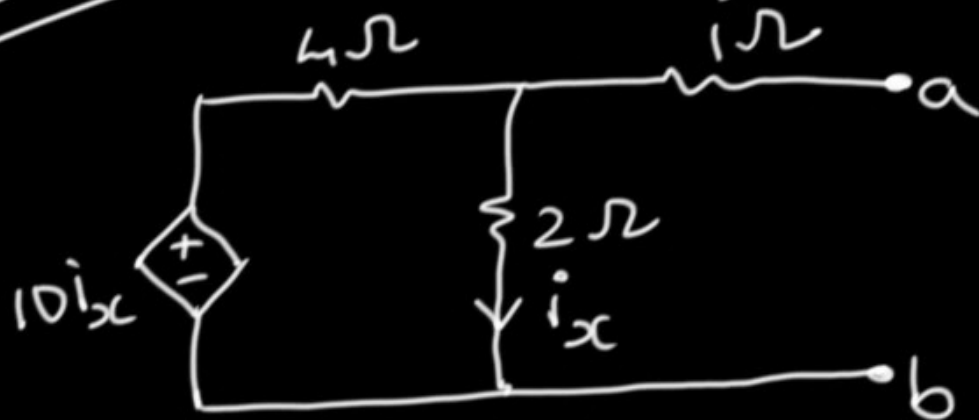

~~a)  $1V, 1\Omega$~~

~~b)  $1V, -1\Omega$~~

c)  $0V, 1\Omega$

d)  $0V, -1\Omega$

KVL-1  $-10i_x - 4(1-i_x) + 2i_x = 0$

$i_x = -1$  (1)

KVL-2  $-2i_x - 1 + V_T = 0 \rightarrow V_T = 1 + 2i_x$  (2)

$$V_T = 1 + 2[-1]$$

$$V_T = -1$$

$$R_{TH} = \frac{V_T}{I} = -1 \underline{\underline{\Omega}}$$

H.W  
GATE/2M.

Find Norton's equivalent  
across X-Y

